
DC Power Transmission


Converters, topologies and load flow


confidential not for public disclosure

AMERICAN TERAWATT

Converter

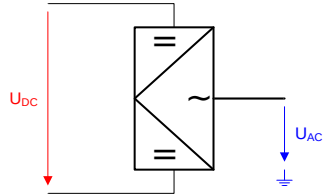

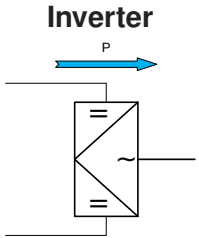


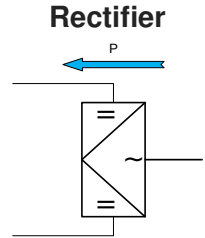

CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE


Converter - Load flow definition

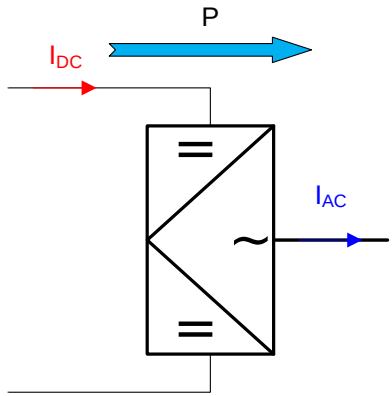- Positive load is defined for the inverter case (generator convention).
- In the USA a common term is “Inverter-Based Resources” (IBR).
- IBR are not only HVDC systems but all kinds of generators:
  - Wind Turbine Generators (WTG)
  - PV, . . .
- A VSC-HVDC system can be an inverter or a rectifier depending on the power-flow direction; some applications require changing direction.



CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE

Converter terminology

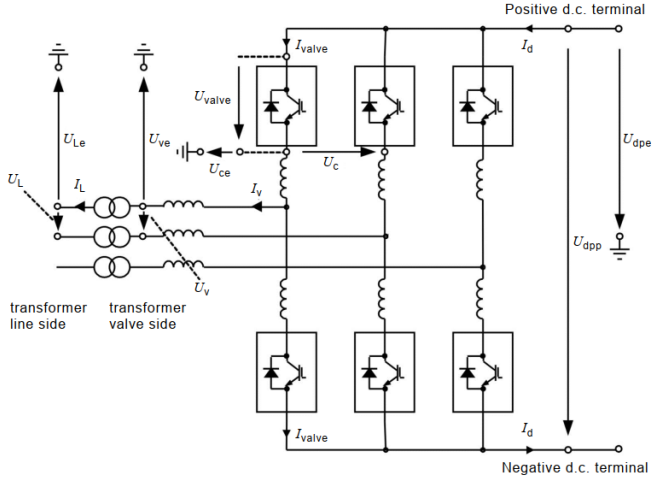


IEC 62747:2014

CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE


DC load flow definitions

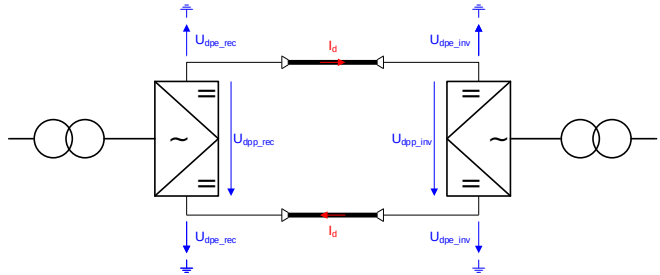- DC equipment (incl. DC line) voltage is defined by the voltages U_{dpe_rec} and U_{dpe_inv}
- Converter size is defined by U_{dpp_rec}
- HVDC systems have bidirectional transmission capability, which means that every individual converter can be either rectifier or inverter



CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE

Monopole

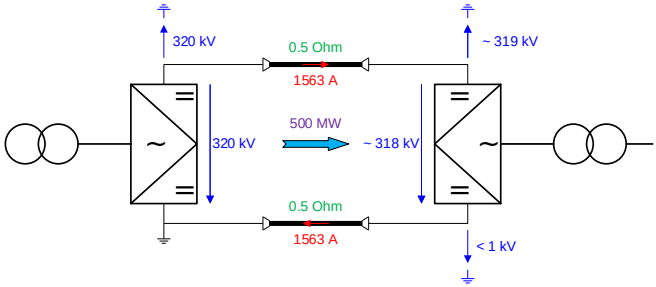

DC load flow

$$U_{dpp_rec} = U_{dpe_rec}$$

$$I_{DC} = \frac{U_{dpp_rec} - U_{dpp_inv}}{2 \cdot R_{DC}}$$


$$U_{dne_rec} = I_d \cdot R_{DC}$$

- Max. voltage created by converter: U_{dpp_rec}
- Max. equipment voltage:
- DC cables have different voltage ratings

CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE


Monopole - extending power transmission

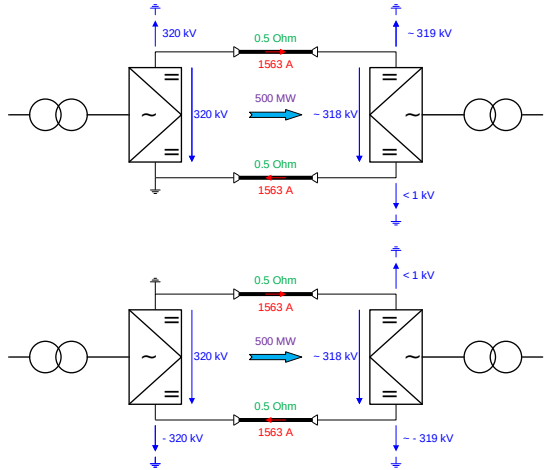- **Higher DC voltage**
  - Limited equipment availability
  - No redundancy
- **Higher DC current**
  - Higher DC line costs
  - No redundancy
- **Additional monopole**
  - Additional converter equipment
  - 4 DC conductors
  - Increased reliability




CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE

Monopole → Bipole (BIP)

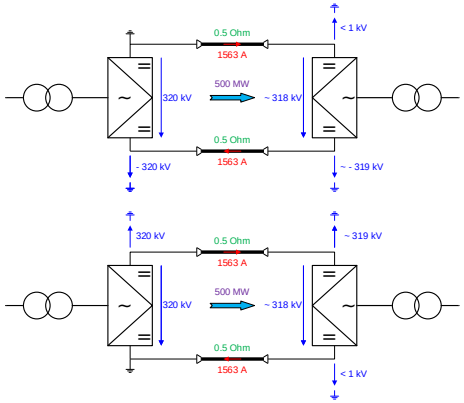


⇒

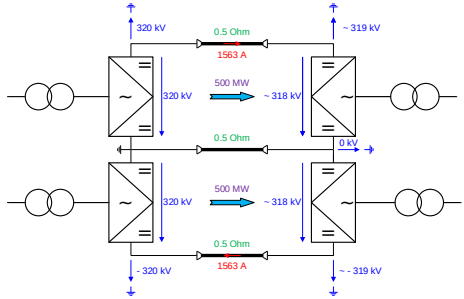

CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE


Bipole (BIP)

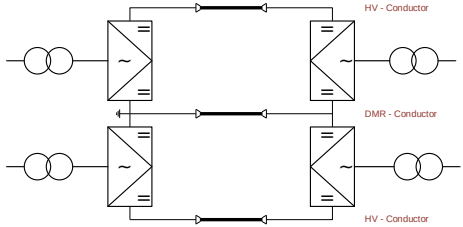- 3 conductors of 2 different types.
- Two poles that can transmit power independently.
- On a fault in one pole, the other pole still transmits power — redundancy.
- In symmetrical operation (both poles equal), no current flows through the DMR.




CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE

BIP operation modes

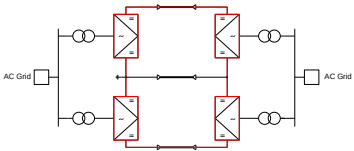


Bipolar — balanced

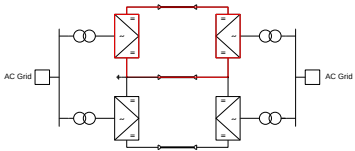- Equal power for poles
- No DMR current
- Loss-optimized



Monopolar

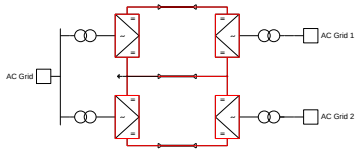- Emergency mode
- System-design definition





Bipolar — unbalanced

- Split-busbar operation
- DMR current flow

CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE

DC load flow

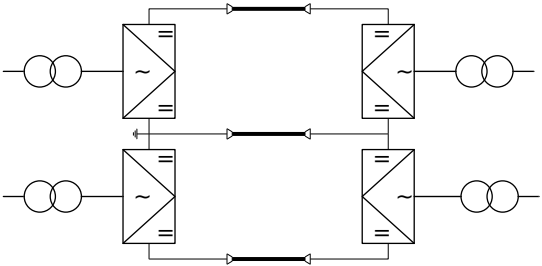


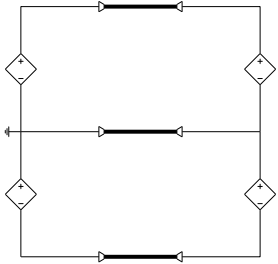

For DC load-flow calculation the converter can be represented as an ideal voltage source.


CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE


Balanced operation

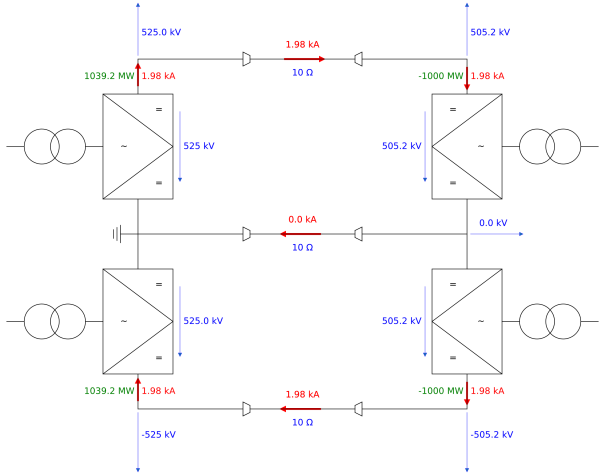

CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE

Balanced operation - power definition

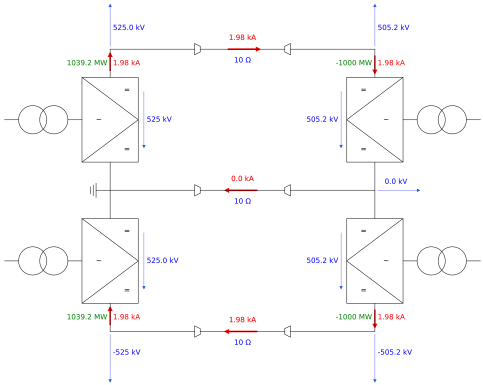


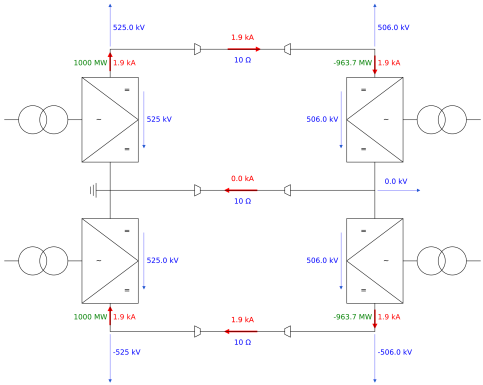


CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE

Balanced vs. unbalanced operation

Balanced mode

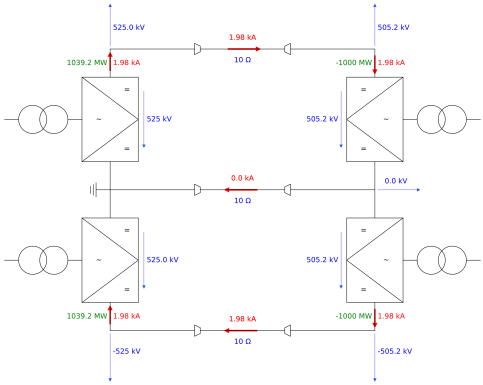


Unbalanced mode

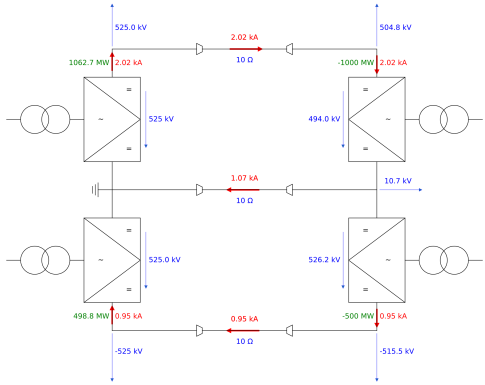

CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE


Monopolar operation

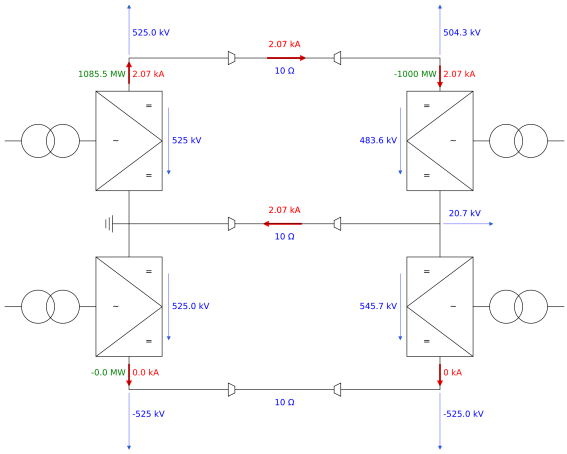


- Usually for a short period, until system reconfiguration is finished.
- For longer operation, the DMR must be designed accordingly.

CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE

System earthing

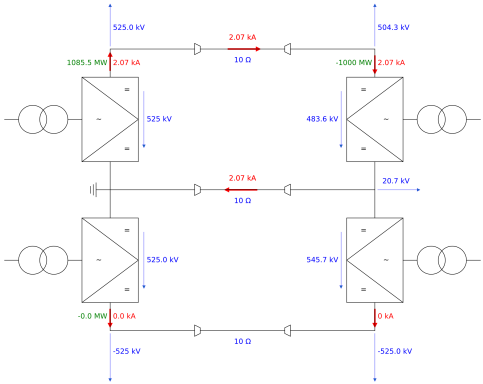


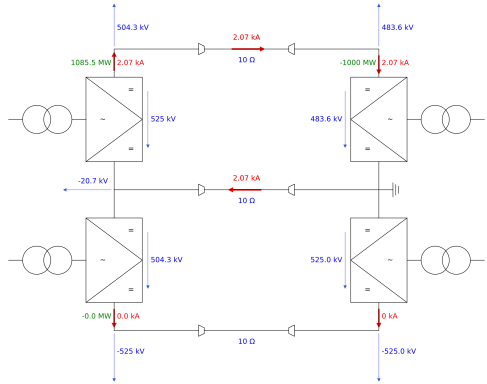


Earthing of the BIP system has no impact on the resulting currents and losses.

CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE

BIP → Rigid BIP

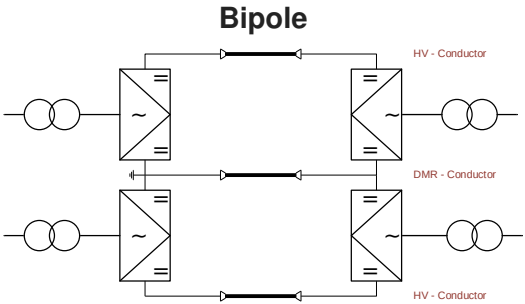


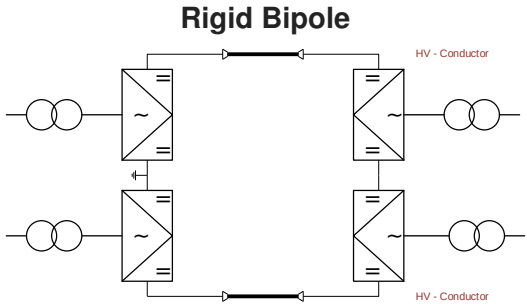

CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE


Rigid BIP

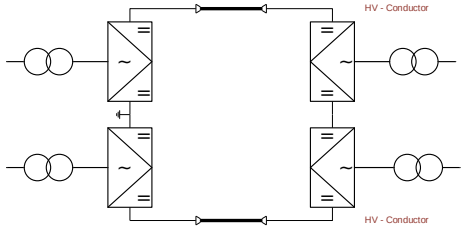- 2 conductors of 1 type.
- Both poles must transmit the same power (same current flows through both poles).
- On a fault in one pole, the other pole might not be able to transmit the power.




CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE

Rigid BIP operation modes

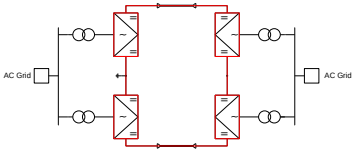


Common-busbar

- Standard operation mode.

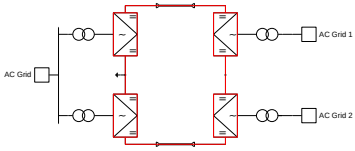

Split-busbar

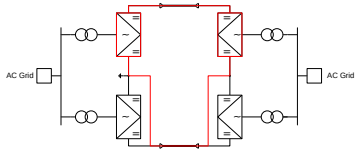- Poles must keep equal power in all modes (incl. dynamic events)




Monopolar

- Reconfiguration takes > 1 s.

CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE

Symmetrical Monopole (SMP)

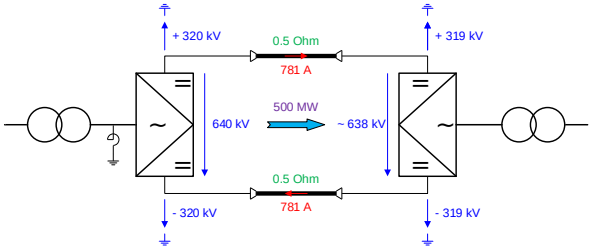

- High-impedance earth reference on the AC side
- $U_{dpp_Rec} = 2 \cdot |U_{dpe_Rec}|$
- $I_d = \frac{U_{dpp_rec} - U_{dpp_inv}}{2 \cdot R_d}$
- Only for VSC-HVDC systems
- DC cables have the same voltage rating

CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE

Modular Multilevel Converter (MMC)

Power transmission parameters:

- Power: 1000 MW
- DC voltage: $\pm$ 320 kV
- Max. DC current: 1563 A


	2 $\times$ Monopole	1 $\times$ BIP	1 $\times$ SMP
Transformers	$--$	$--$	$++$
DC lines	4 lines / 2 types	3 lines / 2 types	2 lines / 1 type
Converters	4 converters	4 converters	2 converters
Converter rating (U_{dpp})	320 kV	320 kV	640 kV
Losses	$--$	$-$	$+$
Reliability	$++$	$+$	$--$

CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE

DC cable

- **Insulator** — XLPE (cross-linked polyethylene) or MI (mass-impregnated).
- **Conductor** — copper or aluminium.
- Balance between DC voltage and DC current for the most economical design.
- Insulator is generally cheaper than conductor $\rightarrow$ higher voltage rating is preferred

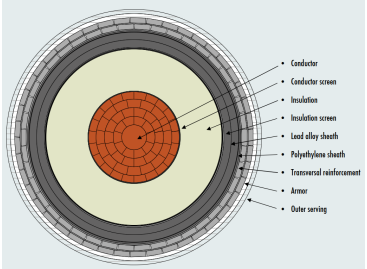Project voltages: 80/200/250/**320**/400/**525** kV (525 kV is new standard for ≥ 2000 MW).





www.borealisgroup.com

CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE

Topology comparison

	Sym. Monopole	Rigid Bipole	Bipole w/ MR
DC conductors	2	2	3
Power on converter fault	0%	50%	50%
Power on DC conductor fault	0%	0%	50%
Economical DC voltage	≤ 400 kV	> 500 kV	> 500 kV
Costs	$	$$	$$$
Max. power	1400 MW (320 kV) 1500 MW (400 kV)	2000 MW	3000 MW

CONFIDENTIAL NOT FOR PUBLIC DISCLOSURE